

# Digital Design & Computer Arch.

## Lecture 5a: Sequential Logic Design II Finite State Machines

Prof. Onur Mutlu

ETH Zürich

Spring 2023

9 March 2023

# First, We Will Complete Sequential Logic Design

# We Covered A Lot of Sequential Logic

---

## ■ Circuits that can store information

- ❑ Cross-coupled inverter
- ❑ R-S Latch
- ❑ Gated D Latch
- ❑ D Flip-Flop
- ❑ Register
- ❑ Memory

## ■ Sequential logic circuits

- ❑ State & Clock
- ❑ Asynchronous vs. Synchronous


## ■ Finite State Machines (FSM)

- ❑ How to design FSMs
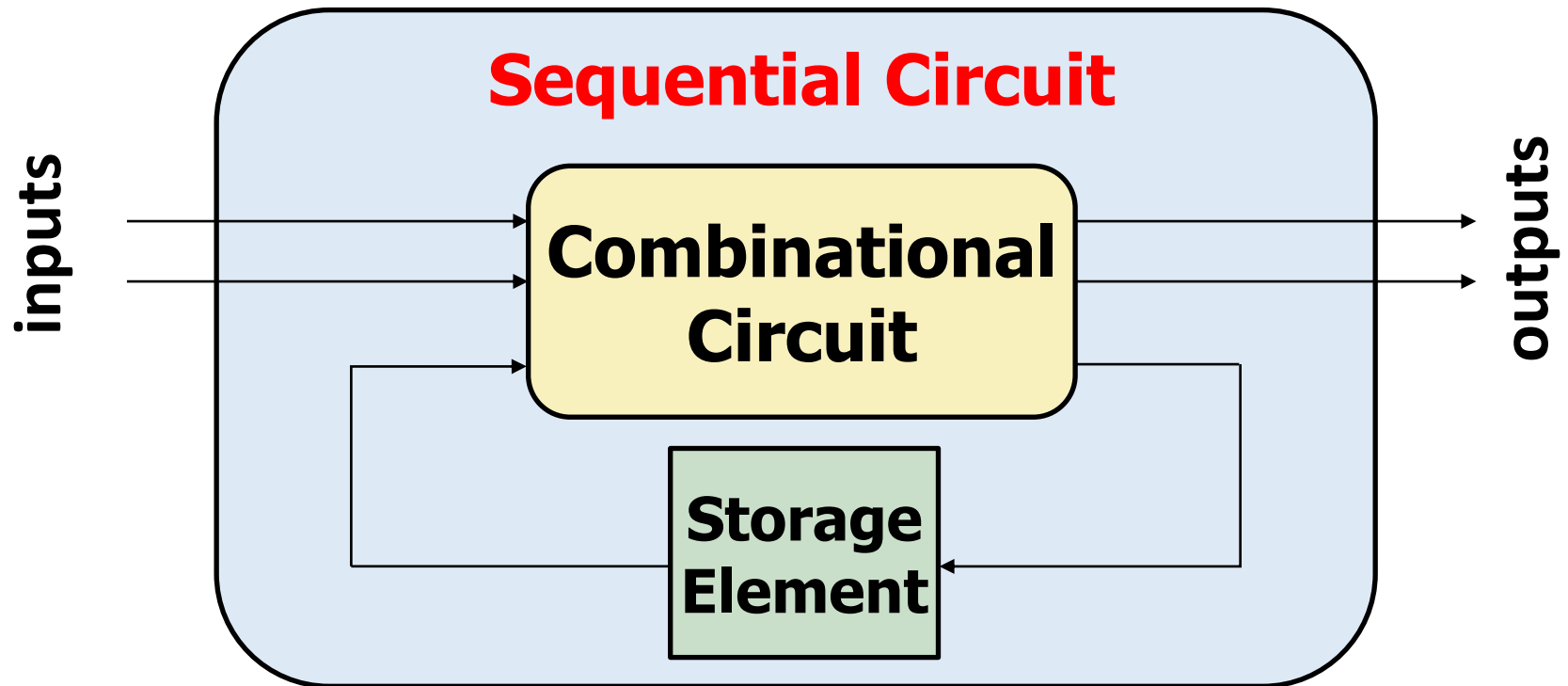
# Recall: Sequential Circuits

---

- Circuits that produce output depending on **current** and **past** input values – circuits with **memory**



# Recall: Sequential Logic Circuits

---



## **Combinational**

Only depends on current inputs




## **Sequential**

Opens depending on past inputs
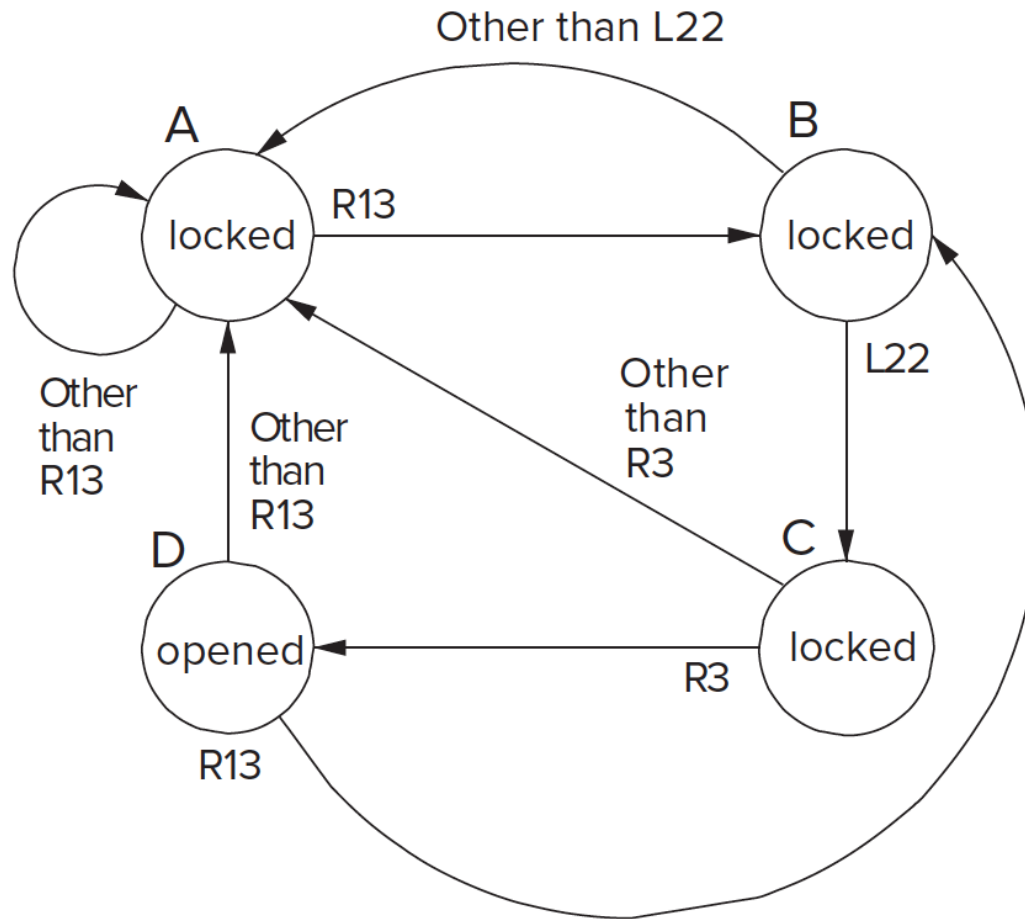
# Recall: State Diagram of Our Sequential Lock

- Completely describes the operation of the sequential lock



# Recall: Finite State Machines (FSMs) Consist of:

---


## ■ Five elements:

1. A **finite** number of **states**
  - **State**: snapshot of all relevant elements of the system at the time of the snapshot
2. A **finite** number of external **inputs**
3. A **finite** number of external **outputs**
4. An explicit **specification of all state transitions**
  - How to get from one state to another
5. An explicit **specification of what determines each external output value**
 
# Recall: Finite State Machines (FSMs)

---

- Each FSM consists of three separate parts:
  - next state logic
  - state register
  - output logic




At the beginning of the clock cycle, next state is latched into the state register



# Recall: Finite State Machines (FSMs) Consist of:


 
## ■ Sequential Circuits

- State register(s)
  - Store the current state and
  - Provide the next state at the clock edge



  
## ■ Combinational Circuits

- Next state logic
  - Determines what the next state will be
- Output logic
  - Generates the outputs



 
# Recall: State Register Implementation

- How can we implement a **state register**? Two properties:
  - We need to store data at the **beginning** of every clock cycle




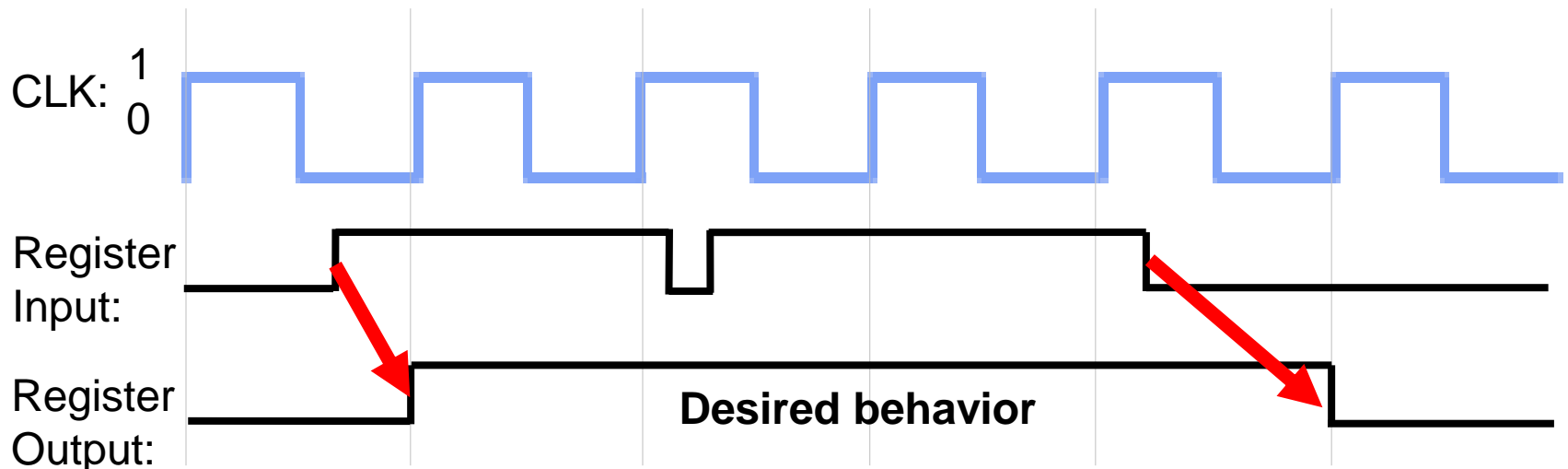- The data must be **available** during the **entire clock cycle**



# Recall: The Problem with Latches: Transparency

Recall the  
Gated D Latch

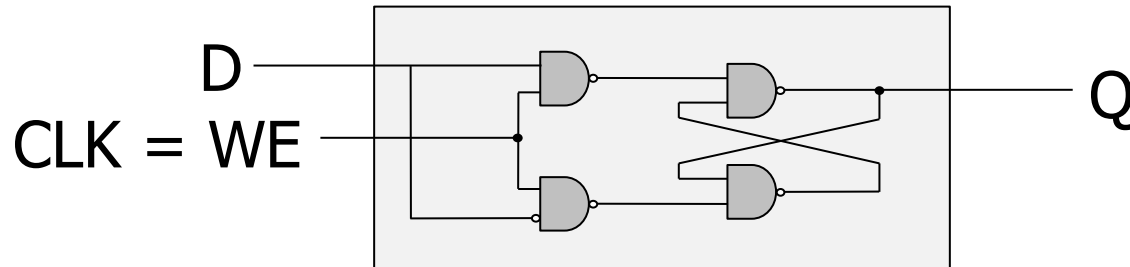


How can we change the latch, so that

**1) D** (input) is **observable** at **Q** (output)  
**only** at the **beginning of next** clock cycle?

**2) Q** is **available for the full clock cycle**

# Recall: The D Flip-Flop

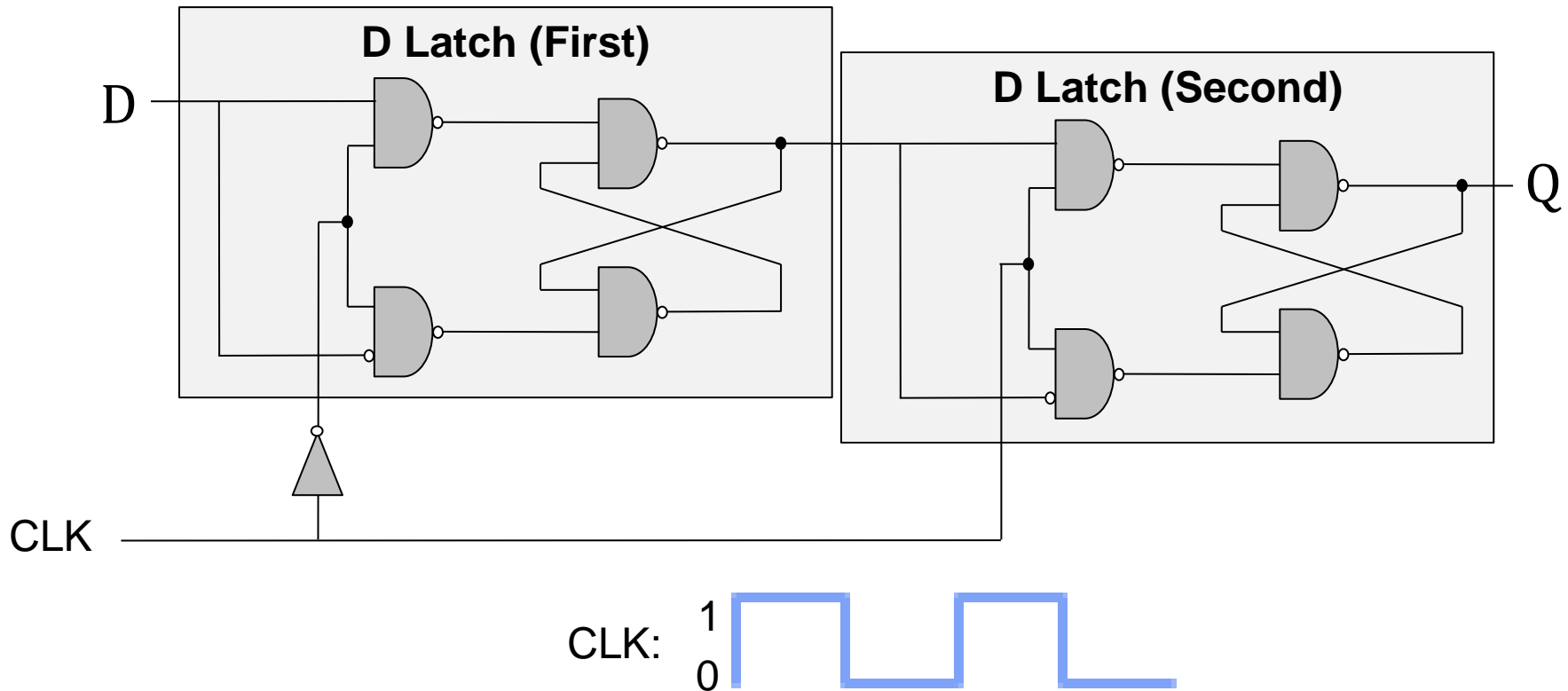- 1) state change on clock edge, 2) data available for full cycle




- When the clock is low, 1<sup>st</sup> latch propagates **D** to the input of the 2<sup>nd</sup> (Q unchanged)
- Only when the clock is high, 2<sup>nd</sup> latch latches **D** (**Q stores D**)
  - At the rising edge of clock (clock going from 0→1), Q gets assigned D

# Recall: The D Flip-Flop

---

 
- 1) state change on clock edge, 2) data available for full cycle



- At the rising edge of clock (clock going from 0->1), **Q** gets assigned **D**
- At all other times, Q is unchanged

# Recall: The D Flip-Flop

 - 1) state change on clock edge, 2) data available for full cycle



We can use **D Flip-Flops**  
to implement the state register

- At the rising edge of clock (clock going from 0->1), **Q** gets assigned **D**
- At all other times, **Q** is unchanged


# Recall: Rising-Clock-Edge Triggered Flip-Flop

---

- **Two inputs:** CLK, D

- **Function**


 
- The flip-flop “samples” **D** on the rising edge of CLK (**positive edge**)
- When CLK rises from 0 to 1, **D** passes through to **Q**
- Otherwise, **Q** holds its previous value
- **Q** changes **only** on the rising edge of CLK



- A flip-flop is called an **edge-triggered state element** because it captures data on the clock edge
  - A latch is a **level-triggered** state element
  
# D Flip-Flop Based Register

- Multiple parallel D flip-flops, each of which storing 1 bit




**This line represents 4 wires**

**This register stores 4 bits**


 
# A 4-Bit D-Flip-Flop-Based Register (Internally)




# Finite State Machines (FSMs)

---

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state


Moore FSM

 


# Finite State Machines (FSMs)

- Next state is determined by the current state and the inputs
- Two types of finite state machines differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state
  - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 


Mealy FSM

 
 
# Finite State Machine Example

- “Smart” traffic light controller
  - **2 inputs:**
    - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - **2 outputs:**
    - Lights:  $L_A$ ,  $L_B$  (Red, Yellow, Green)
  - State can change every 5 seconds
    - Except if green and traffic, stay green




From H&H Section 3.4.1
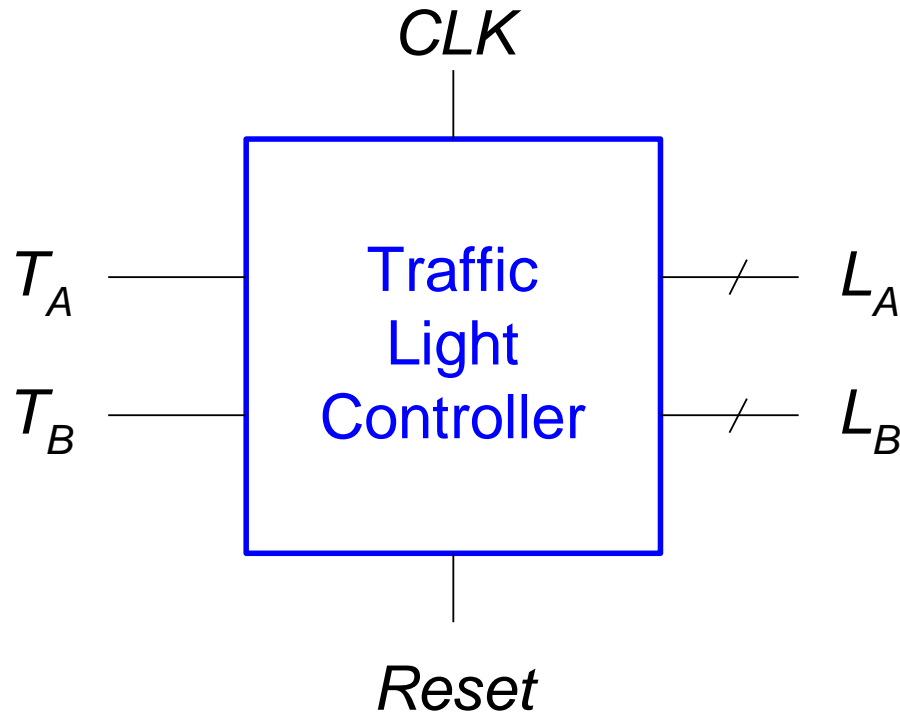
# Finite State Machine Black Box



---

- **Inputs:** CLK, Reset,  $T_A$ ,  $T_B$
- **Outputs:**  $L_A$ ,  $L_B$



 
 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs



 
 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs


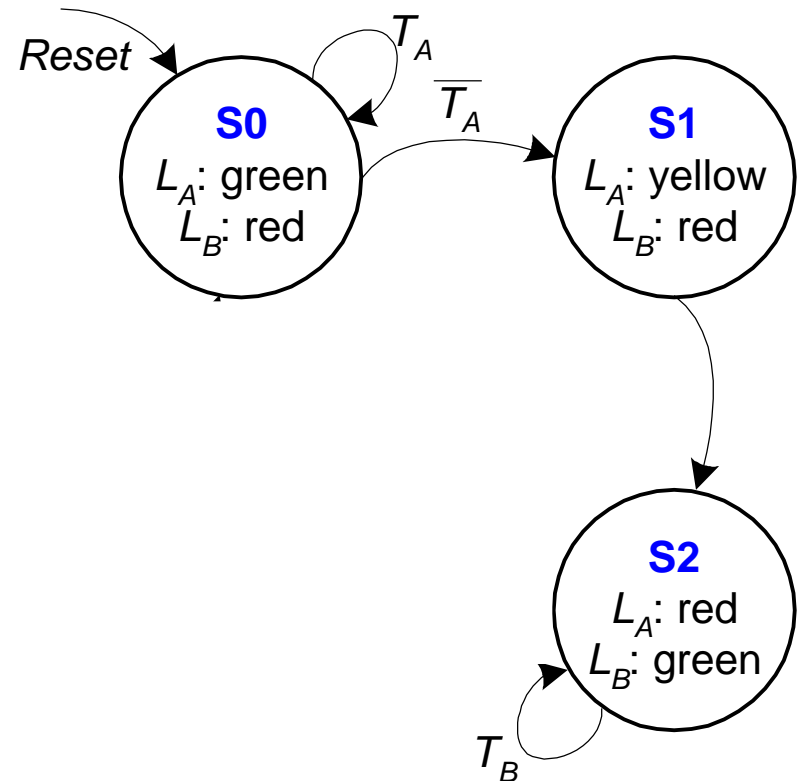 
# Finite State Machine Transition Diagram



- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs





 
 
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs



  
# Finite State Machine Transition Diagram

- **Moore FSM:** outputs labeled in each state
  - **States:** Circles
  - **Transitions:** Arcs




# Finite State Machine: State Transition Table

# FSM State Transition Table

 


Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

# FSM State Transition Table

 

Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0


# FSM State Transition Table

 

Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	00
S1	01
S2	10
S3	11


# FSM State Transition Table

 

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$S'_1 = ?$



# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = ?$$

# FSM State Transition Table

 


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$

# FSM State Transition Table

 

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = S_1 \text{ xor } S_0 \quad \textbf{(Simplified)}$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$


# Finite State Machine: Output Table

# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow


# FSM Output Table

 

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 


$$L_{A1} = S_1$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10



# FSM Output Table

 


$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 


$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1}
 \end{aligned}$$

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM Output Table

 

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1


$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1} \\
 L_{B0} &= S_1 \cdot S_0
 \end{aligned}$$

Output	Encoding
green	00
yellow	01
red	10

# Finite State Machine: Schematic


# FSM Schematic: State Register

---

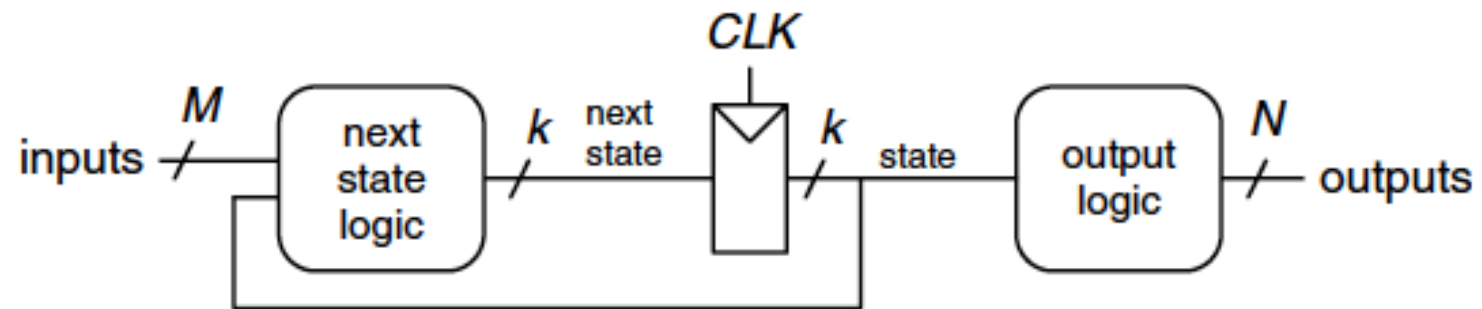


# FSM Schematic: State Register

---

 


# FSM Schematic: Next State Logic

 

$$S'_1 = S_1 \text{ xor } S_0$$

$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$


# FSM Schematic: Output Logic

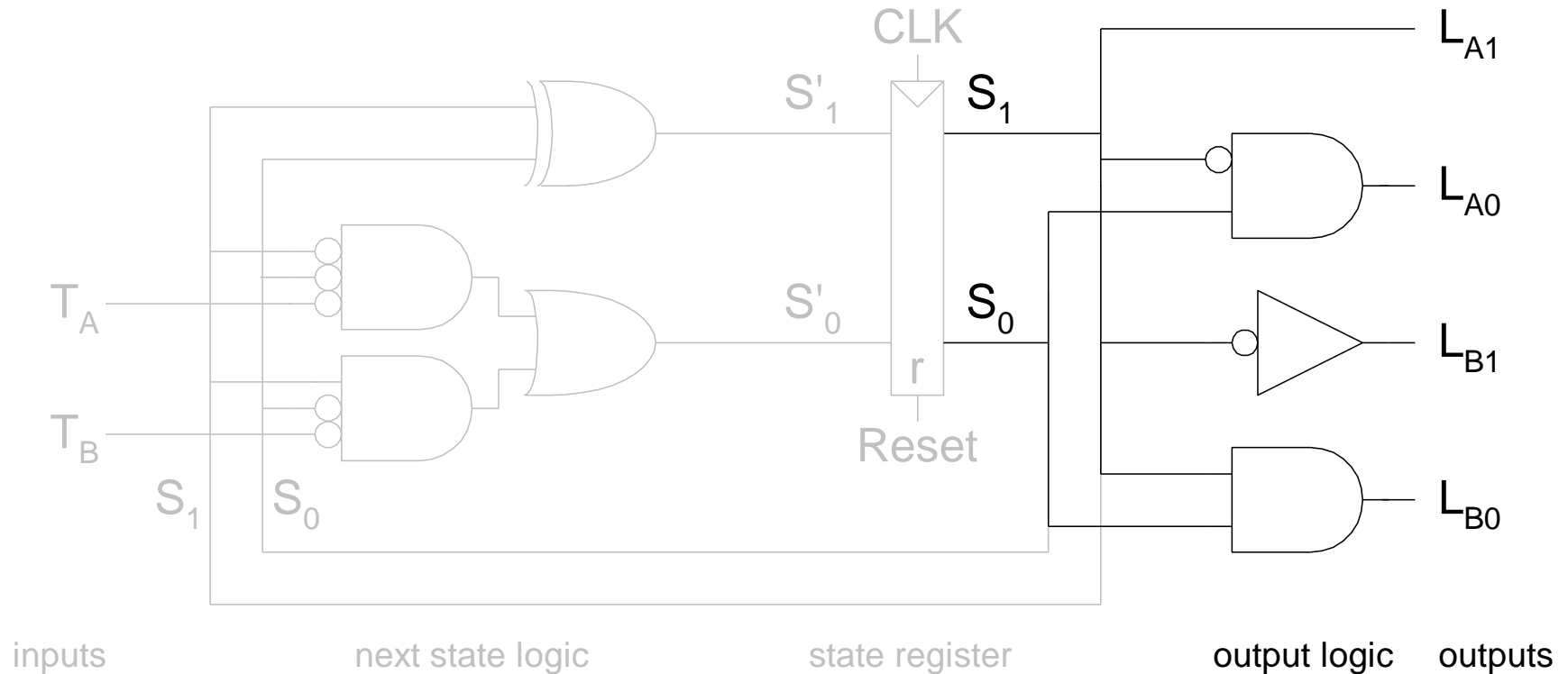

$$\begin{aligned}L_{A1} &= S_1 \\L_{A0} &= \overline{S_1} \cdot S_0 \\L_{B1} &= \overline{S_1} \\L_{B0} &= S_1 \cdot S_0\end{aligned}$$



# FSM Timing Diagram

 

CLK\_

Reset\_

$T_A$  \_

$T_B$  \_



$S'_{1:0}$  \_

$S_{1:0}$  \_



$L_{A1:0}$  \_

$L_{B1:0}$  \_



# FSM Timing Diagram

  



# FSM Timing Diagram

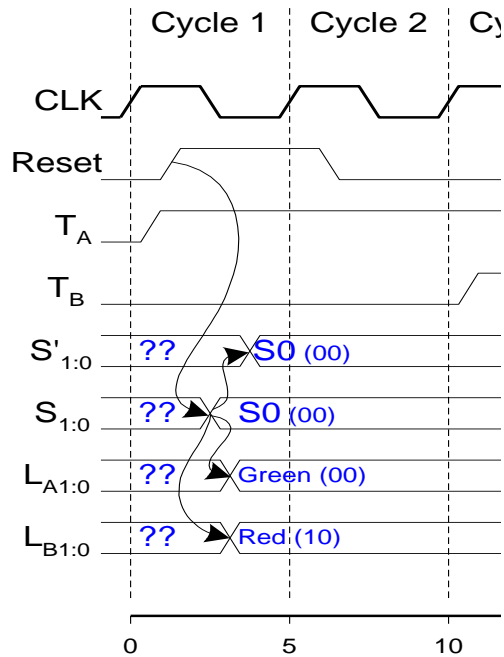 



# FSM Timing Diagram

  



# FSM Timing Diagram

  


# FSM Timing Diagram

  


# FSM Timing Diagram

  

# FSM Timing Diagram


 


This is from H&H Section 3.4.1

 





# FSM Timing Diagram

  

# FSM Timing Diagram

See H&H Chapter 3.4

  


# Finite State Machine: State Encoding
 
# FSM State Encoding

---

- How do we encode the state bits?
  - Three common state binary encodings with different tradeoffs
    1. **Fully Encoded**
    2. **1-Hot Encoded**
    3. **Output Encoded**
- Let's see an example **Swiss** traffic light with 4 states
  - Green, Yellow, Red, Yellow+Red



# FSM State Encoding (II)

---

## 1. Binary Encoding (Full Encoding):

- ❑ Use the minimum possible number of bits
  - Use  $\log_2(num\_states)$  bits to represent the states
- ❑ *Example state encodings: 00, 01, 10, 11*
- ❑ **Minimizes** # flip-flops, but not necessarily output logic or next state logic

## 2. One-Hot Encoding:

- ❑ Each bit encodes a different state
  - Uses  $num\_states$  bits to represent the states
  - Exactly 1 bit is “hot” for a given state
- ❑ *Example state encodings: 0001, 0010, 0100, 1000*
- ❑ **Simplest design process** – very automatable
- ❑ **Maximizes** # flip-flops, **minimizes** next state logic

# FSM State Encoding (III)

---

## 3. Output Encoding:

- ❑ Outputs are **directly accessible** in the state encoding
- ❑ For example, since we have **3 outputs** (light color), encode state with **3 bits**, where each bit represents a color
- ❑ *Example states:* 001, 010, 100, 110
  - Bit<sub>0</sub> encodes **green** light output,
  - Bit<sub>1</sub> encodes **yellow** light output
  - Bit<sub>2</sub> encodes **red** light output
- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines (output function of state)

# FSM State Encoding (III)

---

## 3. Output Encoding:

- ❑ Outputs are **directly accessible** in the state encoding

The **designer** must **carefully** choose an encoding scheme to **optimize** the design under given constraints

- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines (output depends only on state)


# Moore vs. Mealy Machines




# Recall: Moore vs. Mealy FSMs

- Next state is determined by the current state and the inputs
- Two types of FSMs differ in the **output logic**:
  - **Moore FSM**: outputs depend only on the current state
  - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

 



Mealy FSM

 

# Moore vs. Mealy FSM Examples

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.


## Moore FSM

  



# Moore vs. Mealy FSM Examples

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.

Moore FSM

 


Mealy FSM

  



# State Transition Diagrams

Moore FSM

 

What are the tradeoffs?

Mealy FSM

  

# FSM Design Procedure

---

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
  - Generally this is done from a textual description
  - You need to 1) determine the **inputs** and **outputs** for each **state** and 2) figure out how to get from one state to another
- **Approach**
  - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
  - Then continue to add **transitions** and **states**
  - Picking **good state names** is very important
  - Building an FSM is **like** programming (but it *is not* programming!)
    - An FSM has a sequential “control-flow” like a program with conditionals and goto’s
    - The if-then-else construct is controlled by one or more inputs
    - The outputs are controlled by the state or the inputs
  - In hardware, we typically have many concurrent FSMs

# What is to Come: LC-3 Processor

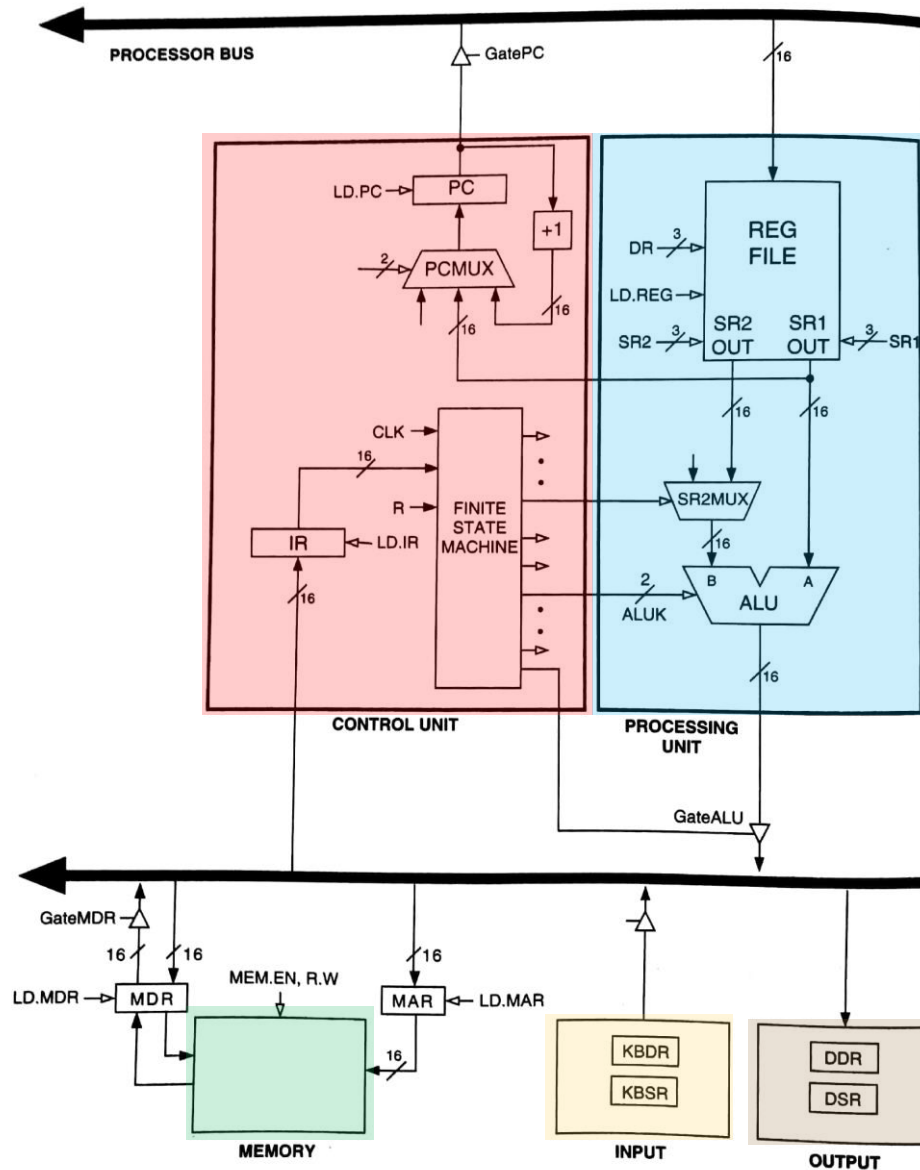


Figure 4.3 The LC-3 as an example of the von Neumann model



# Digital Design & Computer Arch.

## Lecture 5a: Sequential Logic Design II Finite State Machines

Prof. Onur Mutlu

ETH Zürich

Spring 2023

9 March 2023



# Backup Slides: Different Flip-Flop Types

# Enabled Flip-Flops


---

- **Inputs:** CLK, D, EN

- The enable input (EN) controls when new data (D) is stored

- **Function:**

 - **EN = 1:** D passes through to Q on the clock edge
  - **EN = 0:** the flip-flop retains its previous state



# Resettable Flip-Flop

---



- **Inputs:** CLK, D, Reset

- The Reset is used to set the output to 0.

- **Function:**

- **Reset = 1:** Q is forced to 0
  - **Reset = 0:** the flip-flop behaves like an ordinary D flip-flop


## Symbols

  
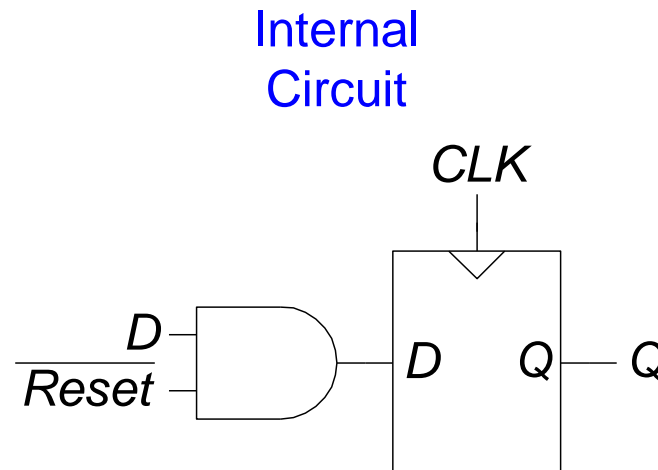
# Resettable Flip-Flops

---

- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when Reset = 1
- Asynchronously resettable flip-flop requires changing the internal circuitry of the flip-flop (see Exercise 3.10)
- Synchronously resettable flip-flop?



# Settable Flip-Flop

---

- **Inputs:** CLK, D, Set
- **Function:**
  - **Set = 1:** Q is set to 1
  - **Set = 0:** the flip-flop behaves like an ordinary D flip-flop

## Symbols

