Digital Design & Computer Arch.

Lab 3 Supplement:
Verilog for Combinational Circuits

Prof. Onur Mutlu

ETH Zurich

Spring 2023

March 2023

What Will We Learn?

- In Lab 3, you will design more combinatorial circuits.

- Convert a binary number to 7-Segment display encoding.

- Implement a circuit to drive the 7-Segment display.

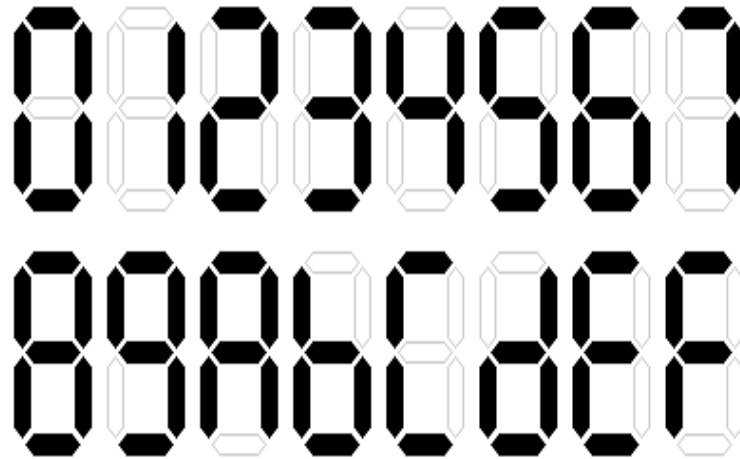- Show the addition result on the 7-Segment display.

7-Segment Display

- A 7-segment display consists of seven separate LEDs in a single package.

- Each of the seven segments is labeled using the letters a, b, c, d, e, f, g.
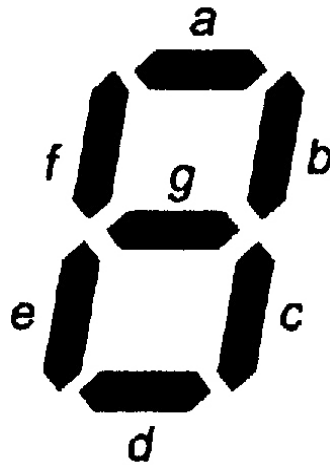
Representing Different Numbers

- We can represent different characters or digits by making particular segments glow at the same time.
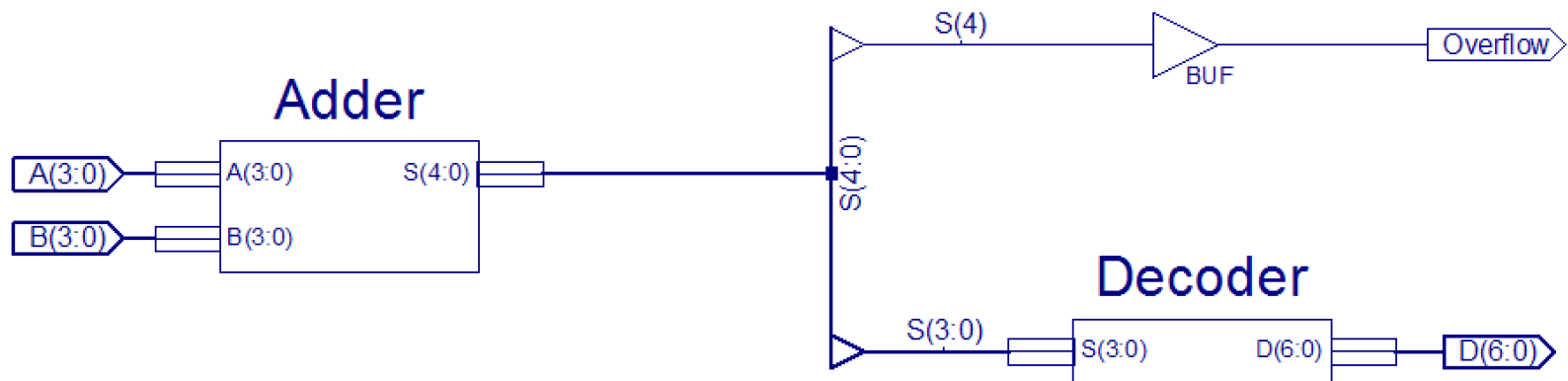
Binary Number to 7-Segment Encoding

- As a first step, you will complete the truth table for converting a 4-bit number to a 7-segment encoding.

- Note: A segment should glow when the corresponding output is logic-0.

Drive the 7-Segment Display

- Design a "decoder" that receives a 4-bit input and returns a 7-bit output signal, and converts a binary number to a 7-segment display encoding.

Show the Results of the Addition

- Show the result of our adder circuit from Lab 2 using the 7-segment display. You need one overflow bit to be displayed on an LED.

- Attach an instance of the decoder to the output of the adder.

- Hint: Create a new "top" module that will create an instance of each module and make appropriate connections between them.

Last Words

- In Lab 3, you will design more combinatorial circuits.

- Convert a binary number to 7-Segment display encoding.

- Implement a circuit to drive the 7-Segment display.

- Show the addition result on the 7-Segment display.

- In the report, you will learn how to display the addition result using only a single 7-segment display.

Report Deadline

23:59, 7 April 2023

Digital Design & Computer Arch.

Lab 3 Supplement:
Verilog for Combinational Circuits

Prof. Onur Mutlu

ETH Zurich

Spring 2023

March 2023